


Name: \_\_\_\_\_

Honor Pledge: I am adhering to the Honor Code while taking this test.

Signature: \_\_\_\_\_

Date: \_\_\_\_\_

 1. The figure shows the simulation of a D flip-flop. **z** is the output.



- A. Which input is normally called "clear" or "reset"? **b**
- B. Why is the value of the output unknown before 10 ns? We are in a "store" state, and we don't know what value is being stored.
- C. If **b** falls to 0 at 68 ns, while **a** remains at 0 and **c** remains at 1, will the output change? **no**
- D. (Five points.) Write a Verilog module (not the test fixture) to implement this circuit.

```
module partF (input a, input b, input c, output reg z);
```

```
always @ (posedge a or posedge b)
```

```
if (b == 1) z <= 0;
```

```
else z <= c;
```

```
endmodule
```

- E. (Two points.) Write a Verilog module to implement a circuit whose output becomes 0 immediately when the clear input goes low (not high); otherwise, the circuit is identical to the previous case.

```
module partF (input a, input b, input c, output reg z);
```

```
always @ (posedge a or negedge b)
```

```
if (b == 0) z <= 0;
```

```
else z <= c;
```

```
endmodule
```

2. Using D flip-flops and logic gates, design a Mealy machine that detects the sequence 1001.

A. First, list all the states ( $s_0, s_1$ , etc.) that we need to define, and briefly define them.


$s_0$ : nothing detected

$s_1$ : first 1 detected

$s_2$ : 10 detected

$s_3$ : 100 detected

 B. (Four points.) Write out the state diagram (not the circuit diagram).



C. How many flip-flops do you need? 2

D. Write out the necessary truth table, showing how Next State and Output depend on Present State and Input.

	q1	q0	In	D1	D0	Out
$s_0$	0	0	0	0	0	0
$s_0$	0	0	1	0	1	0
$s_1$	0	1	0	1	0	0
$s_1$	0	1	1	0	1	0
$s_2$	1	0	0	1	1	0
$s_2$	1	0	1	0	1	0
$s_3$	1	1	0	0	0	0
$s_3$	1	1	1	0	1	1


E. (Three points.) Write a logic equation for each bit's Next State and for the Output.

$$D0 = \sim q1 \& In \mid q1 \& \sim q0 \mid q1 \& q0 \& In$$

$$D1 = \sim In \& (q1 \wedge q0)$$

$$Out = q1 \& q0 \& In$$

 F. (Three points.) Write out the circuit diagram.



G. Write an expression for D0 (as a function of q0, q1, and In) that requires only three logic gates (including NOTs). Your response for part G may be the same as part of your response for part E.

$$D0 = In \mid q1 \& \sim q0$$

H. Write an expression for D1 (as a function of q0, q1, and In) that requires only three logic gates (including NOTs). Your response for part H may be the same as part of your response for part E.

$$D1 = \sim In \& (q1 \wedge q0)$$