


Name: _____

Honor Pledge: I am adhering to the Honor Code while taking this test.

Signature: _____

Date: _____

 1. The figure shows the simulation of a D flip-flop. **z** is the output.



- A. Which input is normally called "clear" or "reset"?
- B. Why is the value of the output unknown before 10 ns?
- C. If **b** falls to 0 at 68 ns, while **a** remains at 0 and **c** remains at 1, will the output change?
- D. (Five points.) Write a Verilog module (not the test fixture) to implement this circuit.
- E. (Two points.) Write a Verilog module to implement a D flip-flop whose output becomes 0 immediately when the clear input goes low (not high); otherwise, the circuit is identical to the previous case.

2. Using D flip-flops and logic gates, design a Mealy machine that detects the sequence 1001.

A. First, list all the states (s_0, s_1 , etc.) that we need to define, and briefly define them.

B. (Four points.) Write out the state diagram (not the circuit diagram).

C. How many flip-flops do you need?

D. Write out the necessary truth table, showing how Next State and Output depend on Present State and Input.

E. (Three points.) Write a logic equation for each bit's Next State and for the Output.

F. (Three points.) Write out the circuit diagram.

G. Write an expression for D_0 (as a function of q_0 , q_1 , and I_n) that requires only three logic gates (including NOTs). Your response for part G may be the same as part of your response for part E.

H. Write an expression for D_1 (as a function of q_0 , q_1 , and I_n) that requires only three logic gates (including NOTs). Your response for part H may be the same as part of your response for part E.